

Jonathan Chu

Name

004832220

EEM16/CSM51A (Fall 2017)

SID #

## Logic Design of Digital Systems

Prof. Ankur Mehta : mehtank@ucla.edu

Problem set 2 | Assigned Monday Oct. 16, 2017  
Show all work. | due 4pm Monday Oct. 30, 2017

### Instructions

This homework is to be done individually. You may consult with others to share thoughts and ideas, but all of your submitted work must be yours alone. Be sure to indicate with whom you've collaborated and in what manner.

You may use any tools or refer to published papers, books, or course notes. You're allowed to make use of online tools such as Logisim, WolframAlpha, etc., provided you properly cite them in the space below.

You must submit this cover sheet plus all pages of your solutions based on the procedure below. Please write early and neatly — if we cannot easily decipher what you have written, you will get zero credit.

### Submission procedure

You need to submit your solution online at Gradescope:

<https://gradescope.com/>

Please see the following guide from Gradescope for submitting homework. You will need to upload a PDF and mark where each question is answered.

[http://gradescope-static-assets.s3-us-west-2.amazonaws.com/help/submitting\\_hw\\_guide.pdf](http://gradescope-static-assets.s3-us-west-2.amazonaws.com/help/submitting_hw_guide.pdf)

### Collaborators

Identify with whom you've collaborated and in what manner, if any.

Angela Wu and Edward Chen went over some answers


### Online resources

Identify which online tools you've used, if any.

None

## EFM16 Part 2

1.1 a)

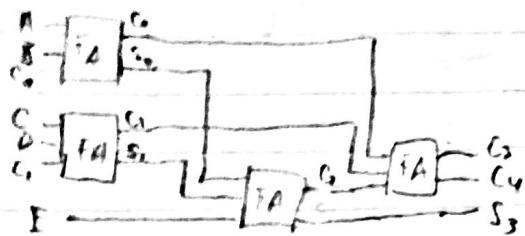

$$\begin{array}{c}
 \begin{array}{c} A \\ + B \\ \hline C_0 \end{array} & \begin{array}{c} C \\ + D \\ \hline C_1 \end{array} \\
 \downarrow & \downarrow \\
 \begin{array}{c} S_0 \\ S_1 \\ \vdots \\ S_4 \end{array} & \begin{array}{c} C_0 \\ C_1 \\ \vdots \\ C_5 \end{array} \\
 \begin{array}{c} E \\ \hline C_2 \\ \hline C_3 S_3 \end{array} & \rightarrow \begin{array}{c} + C_2 \\ \hline C_3 C_4 \end{array} \\
 \downarrow & \downarrow \\
 S_3 C_5 C_4 & 
 \end{array}$$

b) Propagation delay of FAS = maximum of propagation delays of each path to output

$$= \max(6t_{PD}, 9t_{PD}, 3t_{PD}) = 9t_{PD}$$


1.2 a)  $1111 + 1111 + 1111 + 1111 = 11111$

$$= 15 \times 5 = 75 < 127$$

76ns

b)  $A_0 A_1 A_2 A_3 A_4 + B_0 B_1 B_2 B_3 B_4 + \dots + E_0 E_1 E_2 E_3 E_4$


$$= S_0 S_1 S_2 S_3 S_4 S_5 S_6$$

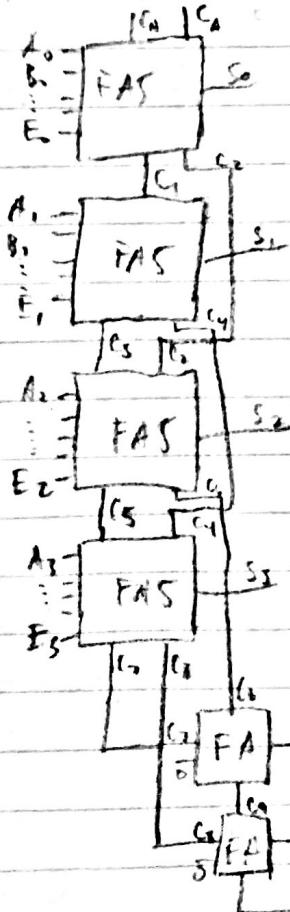

c)  $4(9t_{PD}) + 2(3t_{PD}) = 42t_{PD}$

$4+4+2 = 18$  total FAs

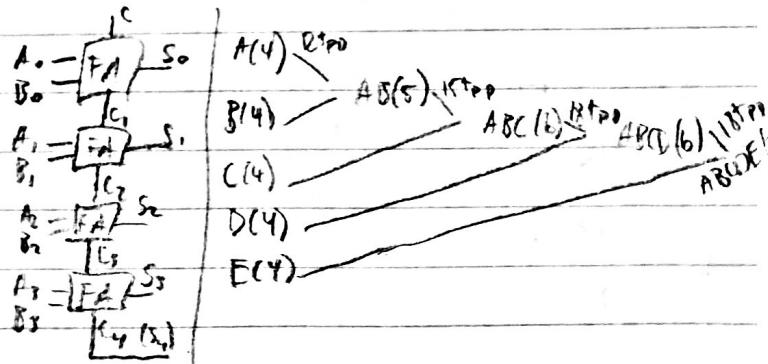d) 2 input 4-bit ripple carry adder. 12t<sub>PD</sub> each



$$(2+15+18+17) = 63t_{PD}$$

$$4+5+6+6 = 21 \text{ FA's}$$

2.1 a)

A,B		E=0					
00	01	11	10	00	01	11	10
00	0	0	0	0	0	0	0
01	1	0	0	0	1	0	0
11	1	1	0	1	1	1	1
10	1	1	0	0	1	1	0

A,B		E=1					
00	01	11	10	00	01	11	10
00	1	0	0	0	1	0	0
01	1	1	0	0	1	1	0
11	1	1	1	1	1	1	1
10	1	1	0	1	1	0	1

$\square = 3D$

$\square = \text{in the page}$

b)  $F = T_1 B_0 \bar{E} + T_1 B_1 + T_1 \bar{T}_0 E + \bar{T}_1 \bar{A}_0 P_0 + B_1 B_0 E + \bar{B}_0 B_1 \bar{E} + A_1 \bar{A}_0 S_1 E$

c) no, it is not benign since the  $A_1 \bar{A}_0 S_1 E$  and  $T_1 \bar{T}_0 E$  implicants are not connected and thus a glitch could result from  $A_1$  changing from high to low.


2.2 a)

2.2g)

$A > B$

$A_1$	$A_0$	$B_1$	$B_0$	$f$
00	x	0	0	0
01	1	x	0	0
11	1	1	x	1
10	.	.	x	0

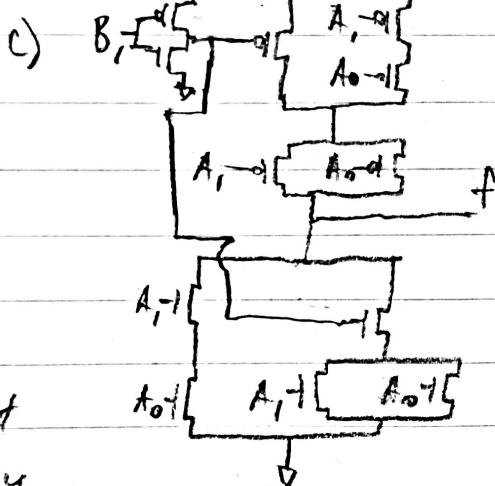b)  $f = A_1 A_0 + A_1 \bar{B}_1 + A_0 \bar{B}_1 = A_1 A_0 + \bar{B}_1 (A_1 + A_0)$




→ This  
K-Map is  $F$ , where

$F=1$  if  $A > B$  and

$F=0$  if  $A < B$ . I have set  
it up this way so that my  
CMOS gate doesn't need to  
be inverted at the end.


2.3  $L = \text{Label}$   $\ell = \text{likelihood}$

a) FCMP2: 2 2-bit inputs

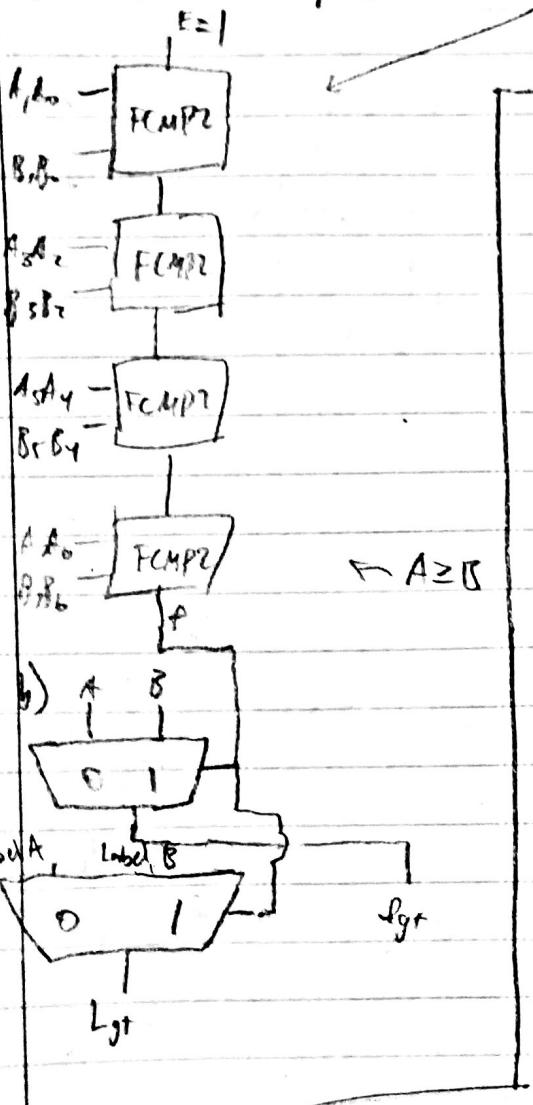

$A_1, A_0, A_3, A_2, A_1, A_0$   
Likelihood of A

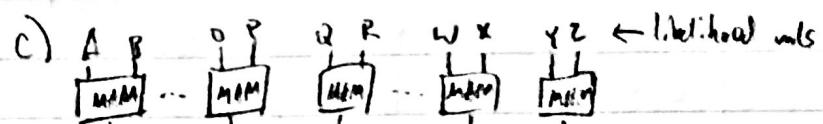$B_1, B_0, B_3, B_4, B_3, B_2, B_1, B_0$   
Likelihood of B



the output we care about  
is likelihood values

$L_{\text{max}}$   $L_{\text{min}}$

5-bit encoding for most likely  
letter

3.1 a) 32 rows (26 letters, 6 dashes)

7 columns (for each segment)

b)	In	Out	In	Out	In	Out	In	Out
A	0x0	0x77	H	0x7	D	0x76	O	0xE
B	0x1	0x7C	I	0x3	P	0xF	V	0x15
C	0x2	0x58	J	0x4	Q	0x1D	W	0x16
D	0x3	0x5E	K	0x1	R	0x11	X	0x17
E	0x4	0x79	L	0x8	S	0x12	Y	0x13
F	0x5	0x71	M	0xL	T	0x13	Z	0x5B
G	0x6	0x6F	N	0xD	U	0x14	0x1A	0x42
				0x54	V	0x3E	0x1F	0x43

3.2 a)  $\boxed{32}$   
b)  $\frac{\text{sg. A}}{1-107}$

$$\frac{G}{1-107}$$

3.2 a) 32

b) 32/A

Letter Decimals

A	0
B	1
C	2
D	3
E	4
F	5
G	6
H	7
I	8
J	9
K	10
L	11
M	12
N	13
O	14
P	15
Q	16
R	17
S	18
T	19
U	20
V	21
W	22
X	23
Y	24
Z	25
	26
	27
	28
	29
	30
	31

$L_4 L_3 L_2 L_1 L_0$

32/G


A	0
B	1
C	2
D	3
E	4
F	5
G	6
H	7
I	8
J	9
K	10
L	11
M	12
N	13
O	14
P	15
Q	16
R	17
S	18
T	19
U	20
V	21
W	22
X	23
Y	24
Z	25
	26
	27
	28
	29
	30
	31

$L_4 L_3 L_2 L_1 L_0$



with 10x40

\* Values in MUX are written in decimal  
to save space/preserve readability

c)

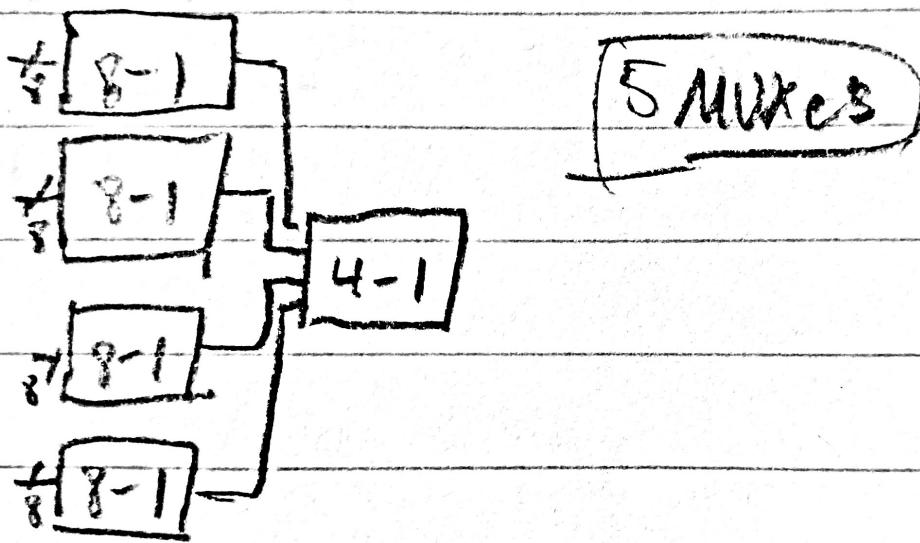

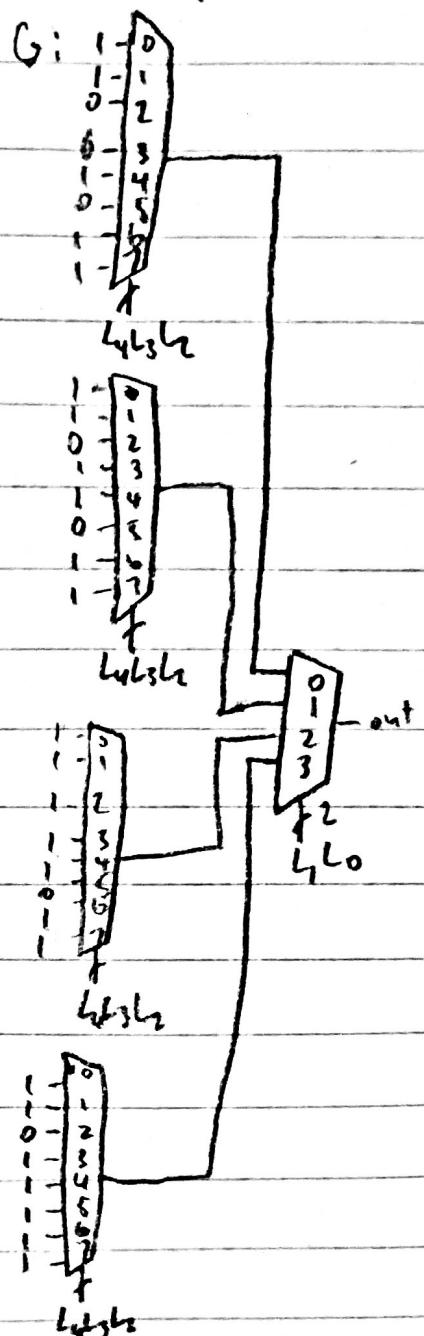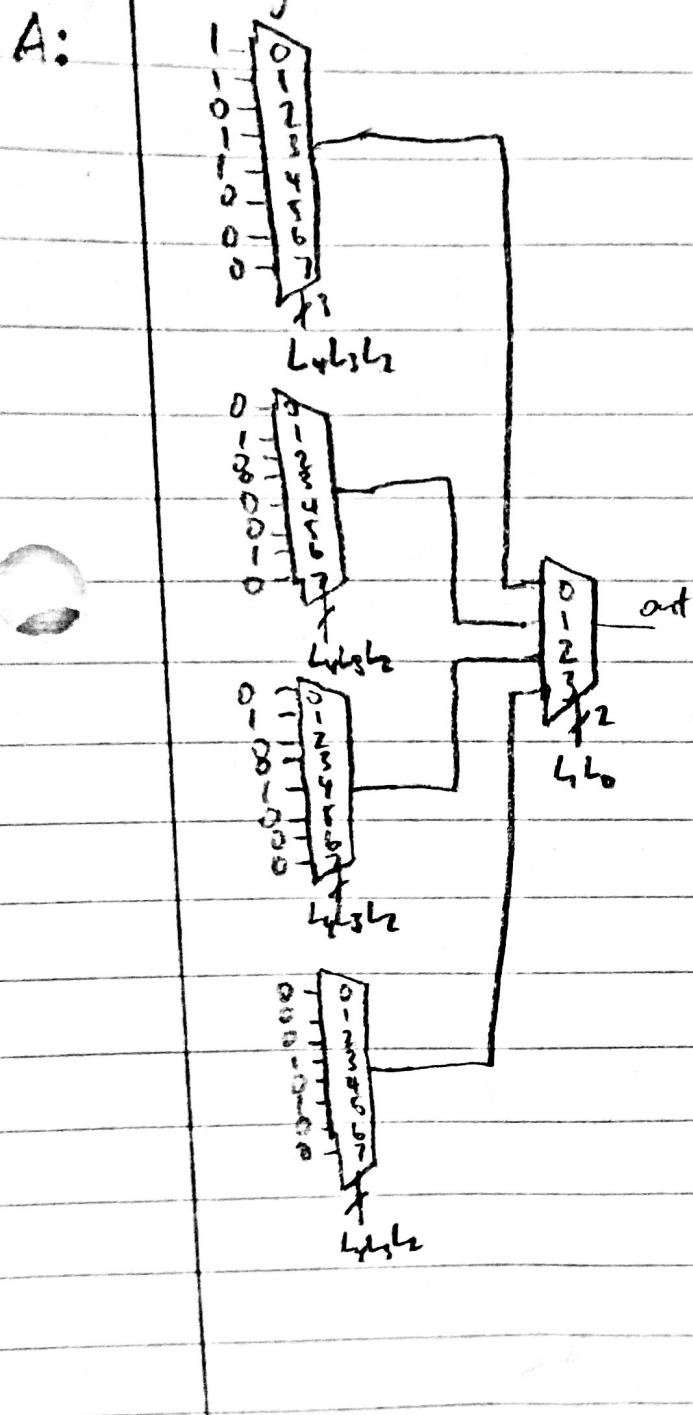d) Again, I will use decimal values in MOXes to save space



Q. I will write this problem on FP/2's complement since all other major topics have been hit hard by these PSE's already.

Consider the following floating point bit representation system FPI:

$\begin{matrix} \text{S} & \text{E} & \text{M} \end{matrix}$

4.1 a) Consider the bits 1000100. Convert this to a decimal value assuming it is a value in:

- i) binary
- ii) hexadecimal
- iii) FPI
- iv) Two's Complement
- v) Signed Magnitude

b) Do the same for the bit string 0101000.

i - v

4.1 b) Give the sum (in decimal) of the answers to (4.1a,iv) and (4.1a,v). Convert it to two's complement and then to signed magnitude.

b) Double your answer to (4.1b,iii) and add it to your answer to (4.1a,v). Explain why it cannot be represented exactly in FPI.

4.1g) i.  $2+8+128 = 138$       10001010

ii.  $16+16^3+16^7$

iii. 0

iv.  $-128+2+8 = -118$

v. -10

b) i.  $8+16+64 = 88$       01011000

ii.  $16^3+16^4+16^6$

iii.  $(1+\frac{1}{16})^{5-3} = (1.0625)^2 = 2.25$

iv. 88

v. 88

4.2g) -128

Two's Complement: 10000000

Signed Magnitude: 110000000

b)  $2.25 \cdot 2 + (-10) = -5.5$

-5.5 cannot be represented in FPI because there do not exist M and E s.t.  $(1+M)^{E-3} = 5.5$ . M is at.f.  $\frac{2^k}{16}$  where  $k \leq 15$ , and there is no M that produces a number raised to an integer power that yields a value with magnitude  $> 5$  and fraction as clean as  $\frac{1}{2}$ .